



# Electricity and Magnetics I

Lecture No.(9)- Semester 1

**Dr. HASSAN M. JABER AL-TA'II**


**Faculty Of Science**

**Al-Muthanna University**

**2017-2018**

## Current and Resistance

Electric currents are flows of electric charge. Suppose a collection of charges is moving perpendicular to a surface of area  $A$ , as shown in Figure 6.1.1.

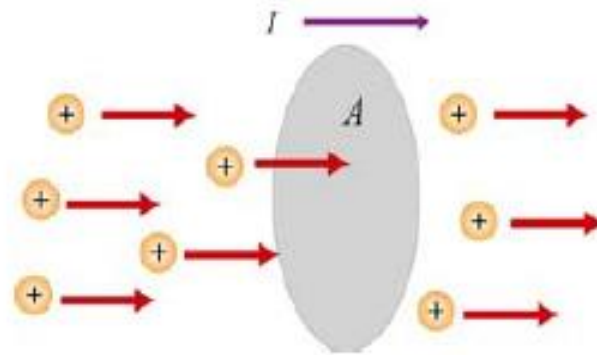

**Figure 6.1.1** Charges moving through a cross section.

The electric current is defined to be the rate at which charges flow across any cross-sectional area. If an amount of charge  $\Delta Q$  passes through a surface in a time interval  $\Delta t$ , then the average current  $I_{\text{avg}}$  is given by

$$I_{\text{avg}} = \frac{\Delta Q}{\Delta t} \quad (6.1.1)$$

The SI unit of current is the ampere (A), with  $1 \text{ A} = 1 \text{ coulomb/sec}$ .

$$I = \frac{dQ}{dt} \quad (6.1.2)$$

Since flow has a direction, we have implicitly introduced a convention that the direction of current corresponds to the direction in which positive charges are flowing. The flowing charges inside wires are negatively charged electrons that move in the opposite direction of the current. Electric currents flow in conductors: solids (metals, semiconductors), liquids (electrolytes, ionized) and gases (ionized), but the flow is impeded in non-conductors or insulators.

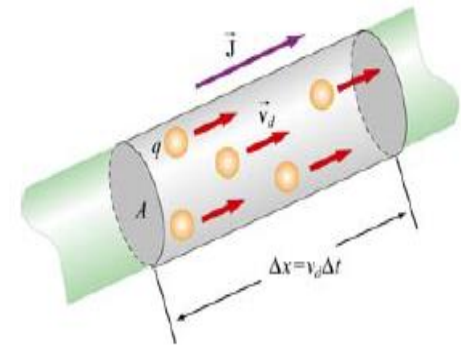



Figure 6.1.2 A microscopic picture of current flowing in a conductor.

$$I = \iint \vec{J} \cdot d\vec{A} \quad (6.1.3)$$

where  $\vec{J}$  is the current density (the SI unit of current density are  $A/m^2$ ). If  $q$  is the charge of each carrier, and  $n$  is the number of charge carriers per unit volume, the total amount of charge in this section is then  $\Delta Q = q(nA \Delta x)$ . Suppose that the charge carriers move with a speed  $v_d$ ; then the displacement in a time interval  $\Delta t$  will be  $\Delta x = v_d \Delta t$ , which implies

$$I_{\text{avg}} = \frac{\Delta Q}{\Delta t} = nq v_d A \quad (6.1.4)$$

The speed  $v_d$  at which the charge carriers are moving is known as the *drift speed*. Physically,  $v_d$  is the average speed of the charge carriers inside a conductor when an external electric field is applied. Actually an electron inside the conductor does not travel in a straight line; instead, its path is rather erratic, as shown in Figure 6.1.3.

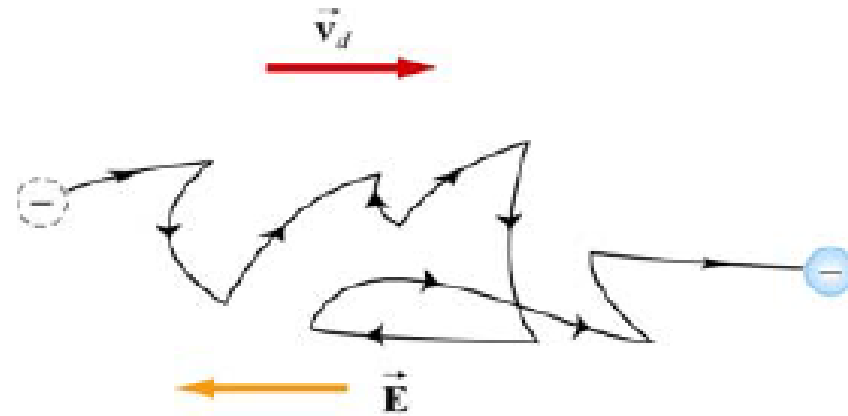

**Figure 6.1.3** Motion of an electron in a conductor.

From the above equations, the current density  $\vec{J}$  can be written as

$$\vec{J} = nq\vec{v}_d \quad (6.1.5)$$

Thus, we see that  $\vec{J}$  and  $\vec{v}_d$  point in the same direction for positive charge carriers, in opposite directions for negative charge carriers.

To find the drift velocity of the electrons, we first note that an electron in the conductor experiences an electric force  $\vec{F}_e = -e\vec{E}$  which gives an acceleration

$$\vec{a} = \frac{\vec{F}_e}{m_e} = -\frac{e\vec{E}}{m_e} \quad (6.1.6)$$

Let the velocity of a given electron immediately after a collision be  $\bar{\mathbf{v}}_i$ . The velocity of the electron immediately before the next collision is then given by

$$\bar{\mathbf{v}}_f = \bar{\mathbf{v}}_i + \bar{\mathbf{a}}t = \bar{\mathbf{v}}_i - \frac{e\bar{\mathbf{E}}}{m_e}t \quad (6.1.7)$$

where  $t$  is the time traveled. The average of  $\bar{\mathbf{v}}_f$  over all time intervals is

$$\langle \bar{\mathbf{v}}_f \rangle = \langle \bar{\mathbf{v}}_i \rangle - \frac{e\bar{\mathbf{E}}}{m_e} \langle t \rangle \quad (6.1.8)$$

which is equal to the drift velocity  $\bar{\mathbf{v}}_d$ . Since in the absence of electric field, the velocity of the electron is completely random, it follows that  $\langle \bar{\mathbf{v}}_i \rangle = 0$ . If  $\tau = \langle t \rangle$  is the average characteristic time between successive collisions (the *mean free time*), we have

$$\bar{\mathbf{v}}_d = \langle \bar{\mathbf{v}}_f \rangle = -\frac{e\bar{\mathbf{E}}}{m_e} \tau \quad (6.1.9)$$

The current density in Eq. (6.1.5) becomes

$$\bar{\mathbf{J}} = -ne\bar{\mathbf{v}}_d = -ne \left( -\frac{e\bar{\mathbf{E}}}{m_e} \tau \right) = \frac{ne^2\tau}{m_e} \bar{\mathbf{E}} \quad (6.1.10)$$

Note that  $\bar{\mathbf{J}}$  and  $\bar{\mathbf{E}}$  will be in the same direction for either negative or positive charge carriers.



## 6.2 Ohm's Law

In many materials, the current density is linearly dependent on the external electric field  $\vec{E}$ . Their relation is usually expressed as


$$\vec{J} = \sigma \vec{E} \quad (6.2.1)$$

where  $\sigma$  is called the *conductivity* of the material. The above equation is known as the (microscopic) Ohm's law. A material that obeys this relation is said to be ohmic; otherwise, the material is non-ohmic.

Comparing Eq. (6.2.1) with Eq. (6.1.10), we see that the conductivity can be expressed as

$$\sigma = \frac{ne^2\tau}{m_e} \quad (6.2.2)$$

To obtain a more useful form of Ohm's law for practical applications, consider a segment of straight wire of length  $l$  and cross-sectional area  $A$ , as shown in Figure 6.2.1.

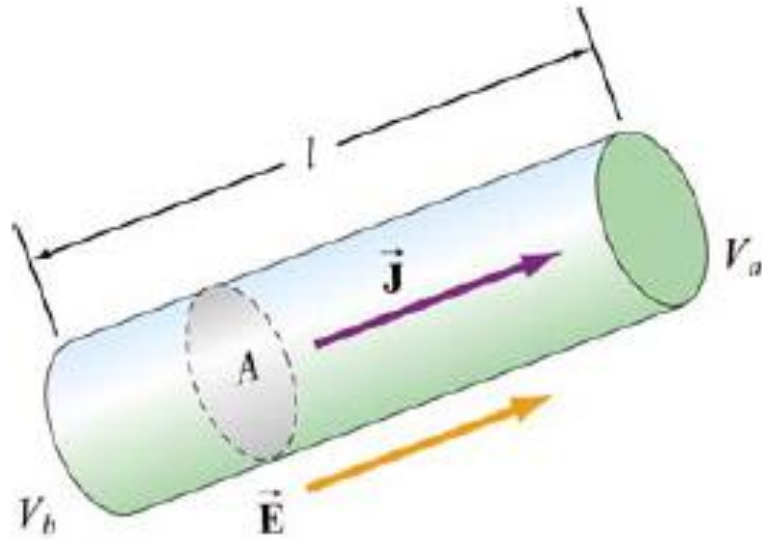

**Figure 6.2.1** A uniform conductor of length  $l$  and potential difference  $\Delta V = V_b - V_a$ .

Suppose a potential difference  $\Delta V = V_b - V_a$  is applied between the ends of the wire, creating an electric field  $\vec{E}$  and a current  $I$ . Assuming  $\vec{E}$  to be uniform, we then have

$$\Delta V = V_b - V_a = -\int_a^b \vec{E} \cdot d\vec{s} = El \quad (6.2.3)$$

The current density can then be written as

$$J = \sigma E = \sigma \left( \frac{\Delta V}{l} \right) \quad (6.2.4)$$

With  $J = I/A$ , the potential difference becomes

$$\Delta V = \frac{l}{\sigma} J = \left( \frac{l}{\sigma A} \right) I = RI \quad (6.2.5)$$

where

$$R = \frac{\Delta V}{I} = \frac{l}{\sigma A} \quad (6.2.6)$$

is the resistance of the conductor. The equation

$$\Delta V = IR \quad (6.2.7)$$

is the “macroscopic” version of the Ohm’s law. The SI unit of  $R$  is the ohm ( $\Omega$ , Greek letter Omega), where

$$1 \Omega \equiv \frac{1 \text{ V}}{1 \text{ A}} \quad (6.2.8)$$

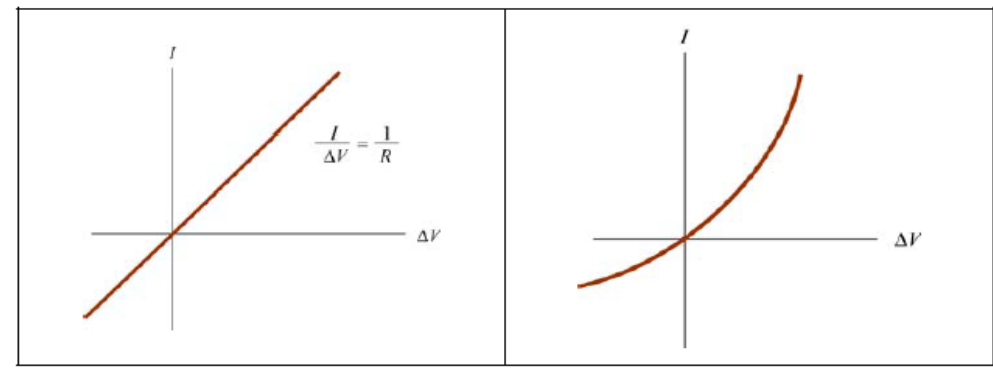


Figure 6.2.2 Ohmic vs. Non-ohmic behavior.

The resistivity  $\rho$  of a material is defined as the reciprocal of conductivity,

$$\rho = \frac{1}{\sigma} = \frac{m_e}{n e^2 \tau} \quad (6.2.9)$$

From the above equations, we see that  $\rho$  can be related to the resistance  $R$  of an object by

$$\rho = \frac{E}{J} = \frac{\Delta V / l}{I / A} = \frac{RA}{l}$$

or

$$R = \frac{\rho l}{A} \quad (6.2.10)$$

The resistivity of a material actually varies with temperature  $T$ . For metals, the variation is linear over a large range of  $T$ :


$$\rho = \rho_0 [1 + \alpha(T - T_0)] \quad (6.2.11)$$

where  $\alpha$  is the *temperature coefficient of resistivity*. Typical values of  $\rho$ ,  $\sigma$  and  $\alpha$  (at  $20^\circ\text{C}$ ) for different types of materials are given in the Table below.

Material	Resistivity $\rho$ ( $\Omega \cdot \text{m}$ )	Conductivity $\sigma$ ( $\Omega \cdot \text{m}$ ) <sup>-1</sup>	Temperature Coefficient $\alpha$ ( $^{\circ}\text{C}$ ) <sup>-1</sup>
<b>Elements</b>			
Silver	$1.59 \times 10^{-8}$	$6.29 \times 10^7$	0.0038
Copper	$1.72 \times 10^{-8}$	$5.81 \times 10^7$	0.0039
Aluminum	$2.82 \times 10^{-8}$	$3.55 \times 10^7$	0.0039
Tungsten	$5.6 \times 10^{-8}$	$1.8 \times 10^7$	0.0045
Iron	$10.0 \times 10^{-8}$	$1.0 \times 10^7$	0.0050
Platinum	$10.6 \times 10^{-8}$	$1.0 \times 10^7$	0.0039
<b>Alloys</b>			
Brass	$7 \times 10^{-8}$	$1.4 \times 10^7$	0.002
Manganin	$44 \times 10^{-8}$	$0.23 \times 10^7$	$1.0 \times 10^{-5}$
Nichrome	$100 \times 10^{-8}$	$0.1 \times 10^7$	0.0004
<b>Semiconductors</b>			
Carbon (graphite)	$3.5 \times 10^{-5}$	$2.9 \times 10^4$	-0.0005
Germanium (pure)	0.46	2.2	-0.048
Silicon (pure)	640	$1.6 \times 10^{-3}$	-0.075
<b>Insulators</b>			
Glass	$10^{10} - 10^{14}$	$10^{-14} - 10^{-10}$	
Sulfur	$10^{15}$	$10^{-15}$	
Quartz (fused)	$7.5 \times 10^{16}$	$1.33 \times 10^{-18}$	

## 6.3 Electrical Energy and Power

Consider a circuit consisting of a battery and a resistor with resistance  $R$  (Figure 6.3.1). Let the potential difference between two points  $a$  and  $b$  be  $\Delta V = V_b - V_a > 0$ . If a charge  $\Delta q$  is moved from  $a$  through the battery, its electric potential energy is increased by  $\Delta U = \Delta q \Delta V$ . On the other hand, as the charge moves across the resistor, the potential energy is decreased due to collisions with atoms in the resistor. If we neglect the internal resistance of the battery and the connecting wires, upon returning to  $a$  the potential energy of  $\Delta q$  remains unchanged.

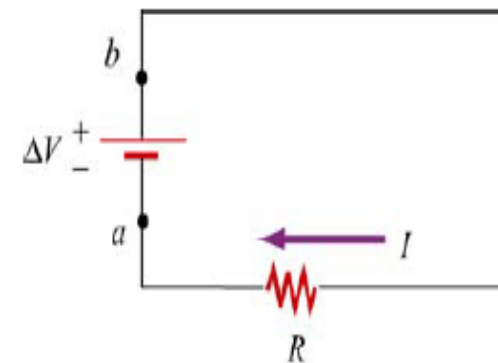

**Figure 6.3.1** A circuit consisting of a battery and a resistor of resistance  $R$ .



Thus, the rate of energy loss through the resistor is given by

$$P = \frac{\Delta U}{\Delta t} = \left( \frac{\Delta q}{\Delta t} \right) \Delta V = I \Delta V \quad (6.3.1)$$

This is precisely the power supplied by the battery. Using  $\Delta V = IR$ , one may rewrite the above equation as

$$\boxed{P = I^2 R = \frac{(\Delta V)^2}{R}} \quad (6.3.2)$$

- The **electric current** is defined as:

$$I = \frac{dQ}{dt}$$

- The **average current** in a conductor is

$$I_{\text{avg}} = nqv_d A$$

where  $n$  is the number density of the charge carriers,  $q$  is the charge each carrier has,  $v_d$  is the **drift speed**, and  $A$  is the cross-sectional area.

- The **current density**  $J$  through the cross sectional area of the wire is

$$\vec{J} = nq\vec{v}_d$$

- Microscopic **Ohm's law**: the current density is proportional to the electric field, and the constant of proportionality is called **conductivity**  $\sigma$  :

$$\vec{J} = \sigma \vec{E}$$

- The reciprocal of conductivity  $\sigma$  is called **resistivity**  $\rho$  :

$$\rho = \frac{1}{\sigma}$$

- Macroscopic Ohm's law: The **resistance**  $R$  of a conductor is the ratio of the potential difference  $\Delta V$  between the two ends of the conductor and the current  $I$ :

$$R = \frac{\Delta V}{I}$$

- Resistance is related to resistivity by

$$R = \frac{\rho l}{A}$$

where  $l$  is the length and  $A$  is the cross-sectional area of the conductor.

- The **drift velocity** of an electron in the conductor is

$$\bar{v}_d = -\frac{e\bar{E}}{m_e} \tau$$

where  $m_e$  is the mass of an electron, and  $\tau$  is the average time between successive collisions.

- The resistivity of a metal is related to  $\tau$  by

$$\rho = \frac{1}{\sigma} = \frac{m_e}{ne^2\tau}$$

- The temperature variation of resistivity of a conductor is

$$\rho = \rho_0 [1 + \alpha (T - T_0)]$$

where  $\alpha$  is the **temperature coefficient of resistivity**.

- **Power**, or rate at which energy is delivered to the resistor is

$$P = I\Delta V = I^2 R = \frac{(\Delta V)^2}{R}$$

### 6.5.1 Resistivity of a Cable

A 3000-km long cable consists of seven copper wires, each of diameter 0.73 mm, bundled together and surrounded by an insulating sheath. Calculate the resistance of the cable. Use  $3 \times 10^{-6} \Omega \cdot \text{cm}$  for the resistivity of the copper.

#### Solution:

The resistance  $R$  of a conductor is related to the resistivity  $\rho$  by  $R = \rho l / A$ , where  $l$  and  $A$  are the length of the conductor and the cross-sectional area, respectively. Since the cable consists of  $N = 7$  copper wires, the total cross sectional area is


$$A = N\pi r^2 = N \frac{\pi d^2}{4} = 7 \frac{\pi (0.073 \text{ cm})^2}{4}$$

The resistance then becomes

$$R = \frac{\rho l}{A} = \frac{(3 \times 10^{-6} \Omega \cdot \text{cm})(3 \times 10^8 \text{ cm})}{7\pi (0.073 \text{ cm})^2 / 4} = 3.1 \times 10^4 \Omega$$

## 6.5.2 Charge at a Junction

Show that the total amount of charge at the junction of the two materials in Figure 6.5.1 is  $\epsilon_0 I (\sigma_2^{-1} - \sigma_1^{-1})$ , where  $I$  is the current flowing through the junction, and  $\sigma_1$  and  $\sigma_2$  are the conductivities for the two materials.

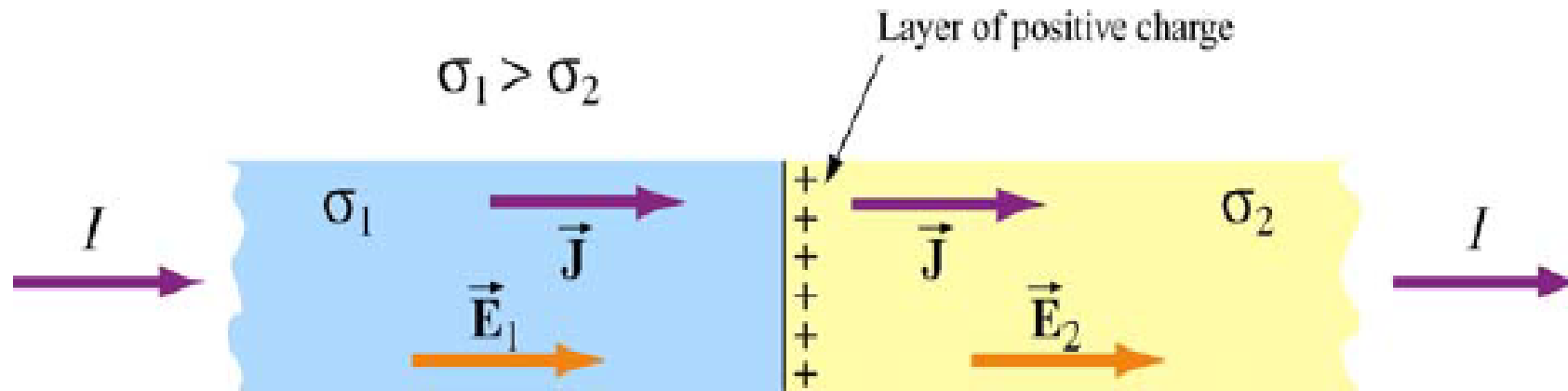

**Figure 6.5.1** Charge at a junction.



## Solution:

In a steady state of current flow, the normal component of the current density  $\vec{J}$  must be the same on both sides of the junction. Since  $J = \sigma E$ , we have  $\sigma_1 E_1 = \sigma_2 E_2$

or

$$E_2 = \left( \frac{\sigma_1}{\sigma_2} \right) E_1$$

Let the charge on the interface be  $q_{\text{in}}$ , we have, from the Gauss's law:

$$\oiint_S \vec{E} \cdot d\vec{A} = (E_2 - E_1) A = \frac{q_{\text{in}}}{\epsilon_0}$$

or

$$E_2 - E_1 = \frac{q_{\text{in}}}{A\epsilon_0}$$

Substituting the expression for  $E_2$  from above then yields

$$q_{\text{in}} = \epsilon_0 A E_1 \left( \frac{\sigma_1}{\sigma_2} - 1 \right) = \epsilon_0 A \sigma_1 E_1 \left( \frac{1}{\sigma_2} - \frac{1}{\sigma_1} \right)$$

Since the current is  $I = JA = (\sigma_1 E_1) A$ , the amount of charge on the interface becomes

$$q_{\text{in}} = \epsilon_0 I \left( \frac{1}{\sigma_2} - \frac{1}{\sigma_1} \right)$$

### 6.5.3 Drift Velocity

The resistivity of seawater is about  $25 \Omega \cdot \text{cm}$ . The charge carriers are chiefly  $\text{Na}^+$  and  $\text{Cl}^-$  ions, and of each there are about  $3 \times 10^{20} / \text{cm}^3$ . If we fill a plastic tube 2 meters long with seawater and connect a 12-volt battery to the electrodes at each end, what is the resulting average drift velocity of the ions, in cm/s?

#### **Solution:**

The current in a conductor of cross sectional area  $A$  is related to the drift speed  $v_d$  of the charge carriers by

$$I = enAv_d$$

where  $n$  is the number of charges per unit volume. We can then rewrite the Ohm's law as

$$V = IR = (neAv_d) \left( \frac{\rho l}{A} \right) = nev_d \rho l$$

which yields

$$v_d = \frac{V}{ne\rho l}$$

Substituting the values, we have


$$v_d = \frac{12\text{V}}{(6 \times 10^{20}/\text{cm}^3)(1.6 \times 10^{-19}\text{C})(25\Omega \cdot \text{cm})(200\text{cm})} = 2.5 \times 10^{-5} \frac{\text{V} \cdot \text{cm}}{\text{C} \cdot \Omega} = 2.5 \times 10^{-5} \frac{\text{cm}}{\text{s}}$$

In converting the units we have used

$$\frac{\text{V}}{\Omega \cdot \text{C}} = \left( \frac{\text{V}}{\Omega} \right) \frac{1}{\text{C}} = \frac{\text{A}}{\text{C}} = \text{s}^{-1}$$

### 6.5.5 Resistance of a Hollow Cylinder

Consider a hollow cylinder of length  $L$  and inner radius  $a$  and outer radius  $b$ , as shown in Figure 6.5.3. The material has resistivity  $\rho$ .

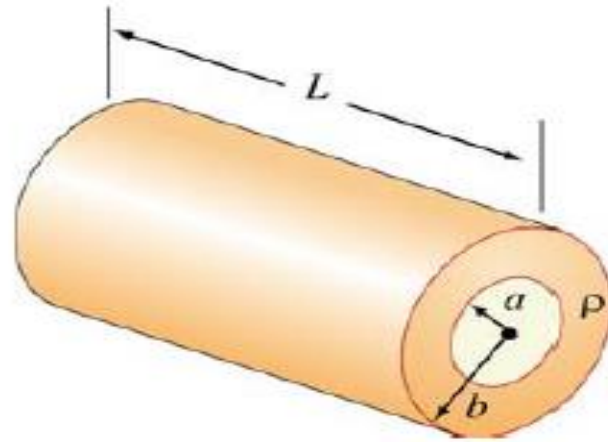

**Figure 6.5.3** A hollow cylinder.

- (a) Suppose a potential difference is applied between the ends of the cylinder and produces a current flowing parallel to the axis. What is the resistance measured?
- (b) If instead the potential difference is applied between the inner and outer surfaces so that current flows radially outward, what is the resistance measured?

## Solution:

(a) When a potential difference is applied between the ends of the cylinder, current flows parallel to the axis. In this case, the cross-sectional area is  $A = \pi(b^2 - a^2)$ , and the resistance is given by

$$R = \frac{\rho L}{A} = \frac{\rho L}{\pi(b^2 - a^2)}$$

(b) Consider a differential element which is made up of a thin cylinder of inner radius  $r$  and outer radius  $r + dr$  and length  $L$ . Its contribution to the resistance of the system is given by

$$dR = \frac{\rho dl}{A} = \frac{\rho dr}{2\pi rL}$$

where  $A = 2\pi rL$  is the area normal to the direction of current flow. The total resistance of the system becomes

$$R = \int_a^b \frac{\rho dr}{2\pi rL} = \frac{\rho}{2\pi L} \ln\left(\frac{b}{a}\right)$$

## Homework

**Q1/** A sphere of radius 10 mm that carries a charge of  $8 \text{ nC} = 8 \times 10^{-9} \text{ C}$  is whirled in a circle at the end of an insulated string. The rotation frequency is  $100\pi \text{ rad/s}$ .

- (a) What is the basic definition of current in terms of charge?
- (b) What average current does this rotating charge represent?
- (c) What is the average current density over the area traversed by the sphere?

**Q2/** A 1500 W radiant heater is constructed to operate at 115 V.


- (a) What will be the current in the heater? [Ans.  $\sim 10 \text{ A}$ ]
- (b) What is the resistance of the heating coil? [Ans.  $\sim 10 \Omega$ ]
- (c) How many kilocalories are generated in one hour by the heater? (1 Calorie = 4.18 J)

- Q3/** A wire with a resistance of  $6.0 \Omega$  is drawn out through a die so that its new length is three times its original length. Find the resistance of the longer wire, assuming that the resistivity and density of the material are not changed during the drawing process. [Ans:  $54 \Omega$ ].
- Q4/** A 100-W light bulb is plugged into a standard 120-V outlet. (a) How much does it cost per month (31 days) to leave the light turned on? Assume electricity costs 6 cents per  $\text{kW} \cdot \text{h}$ . (b) What is the resistance of the bulb? (c) What is the current in the bulb? [Ans: (a) \$4.46; (b)  $144 \Omega$ ; (c)  $0.833 \text{ A}$ ].



Q5/

Figure 6.7.3 shows a three-layer sandwich made of two resistive materials with resistivities  $\rho_1$  and  $\rho_2$ . From left to right, we have a layer of material with resistivity  $\rho_1$  of width  $d/3$ , followed by a layer of material with resistivity  $\rho_2$ , also of width  $d/3$ , followed by another layer of the first material with resistivity  $\rho_1$ , again of width  $d/3$ .

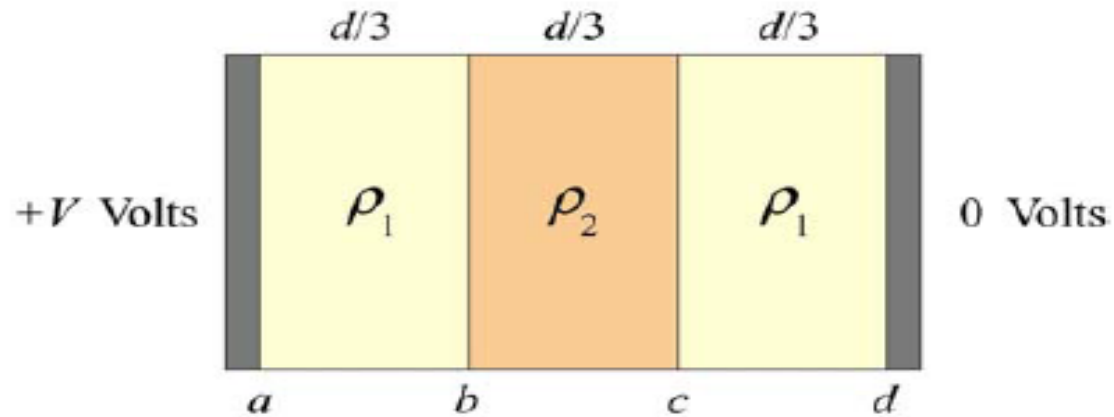

**Figure 6.7.3** Charge accumulation at interface.

There are four interfaces between the various materials and the conductors, which we label  $a$  through  $d$ , as indicated on the sketch. A steady current  $I$  flows through this sandwich from left to right, corresponding to a current density  $J = I/A$ .

(a) What are the electric fields  $\vec{E}_1$  and  $\vec{E}_2$  in the two different dielectric materials? To obtain these fields, assume that the current density is the same in every layer. Why must this be true? [Ans: All fields point to the right,  $E_1 = \rho_1 I/A$ ,  $E_2 = \rho_2 I/A$ ; the current densities must be the same in a steady state, otherwise there would be a continuous buildup of charge at the interfaces to unlimited values.]

(b) What is the total resistance  $R$  of this sandwich? Show that your expression reduces to the expected result if  $\rho_1 = \rho_2 = \rho$ . [Ans:  $R = d(2\rho_1 + \rho_2)/3A$ ; if  $\rho_1 = \rho_2 = \rho$ , then  $R = d\rho/A$ , as expected.]

(c) As we move from right to left, what are the changes in potential across the three layers, in terms of  $V$  and the resistivities? [Ans:  $V\rho_1/(2\rho_1 + \rho_2)$ ,  $V\rho_2/(2\rho_1 + \rho_2)$ ,  $V\rho_1/(2\rho_1 + \rho_2)$ , summing to a total potential drop of  $V$ , as required].

(d) What are the charges per unit area,  $\sigma_a$  through  $\sigma_d$ , at the interfaces? Use Gauss's Law and assume that the electric field in the conducting caps is zero. [Ans:  $\sigma_a = -\sigma_d = 3\varepsilon_0 V \rho_1 / d(2\rho_1 + \rho_2)$ ,  $\sigma_b = -\sigma_c = 3\varepsilon_0 V (\rho_2 - \rho_1) / d(2\rho_1 + \rho_2)$ .]

(e) Consider the limit  $\rho_2 \gg \rho_1$ . What do your answers above reduce to in this limit?